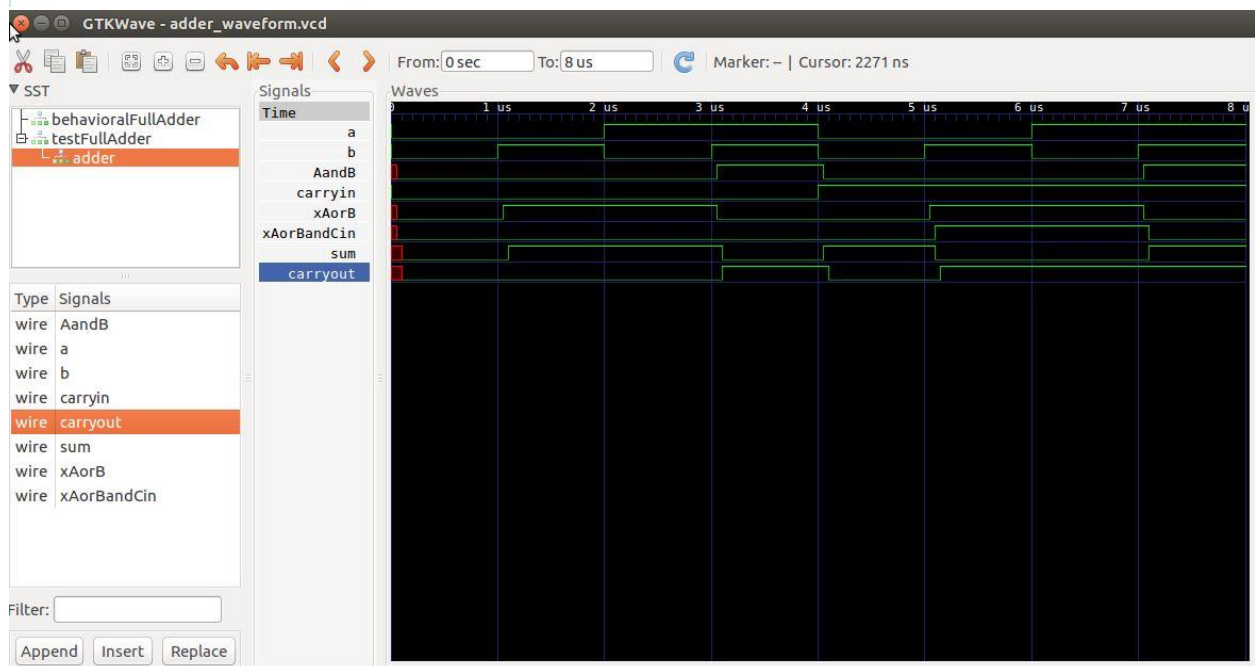


# Lauren Pudvan

## HW2

### Adder


```
comparch@comparchVM:~/comparch/HW2$ iverilog -o adder adder.t.v
./adder.v:8: warning: timescale for behavioralFullAdder inherited from another file.
adder.t.v:2: ...: The inherited timescale is here.
./adder.v:20: warning: timescale for structuralFullAdder inherited from another file.
adder.t.v:2: ...: The inherited timescale is here.
comparch@comparchVM:~/comparch/HW2$ ./adder
a b carryin | sum carryout | Exp Sum Exp Cout
0 0 0       | 0 0           | 0 0 0 0
0 1 0       | 1 0           | 1 0 0 0
1 0 0       | 1 0           | 1 0 0 0
1 1 0       | 0 1           | 0 1 0 1
0 0 1       | 1 0           | 1 0 0 0
0 1 1       | 0 1           | 0 1 0 1
1 0 1       | 1 0           | 1 0 0 1
1 1 1       | 1 1           | 1 1 0 1
comparch@comparchVM:~/comparch/HW2$ gtkwave adder_waveform.vcd
```



The expected outputs match the actual outputs. The adder is adding the bits and providing a carryover if necessary!

## Decoder

```
comparch@comparchVM:~/comparch/Hw2$ iverilog -o decoder decoder.t.v
./decoder.v:7: warning: timescale for behavioralDecoder inherited from another file.
decoder.t.v:2: ...: The inherited timescale is here.
./decoder.v:18: warning: timescale for structuralDecoder inherited from another file.
decoder.t.v:2: ...: The inherited timescale is here.
comparch@comparchVM:~/comparch/Hw2$ ./decoder
En A0 A1 | 00 01 02 03 | Expected output
0 0 0 | 0 0 0 0 | All false
0 1 0 | 0 0 0 0 | All false
0 0 1 | 0 0 0 0 | All false
0 1 1 | 0 0 0 0 | All false
1 0 0 | 1 0 0 0 | 00 only
1 1 0 | 0 1 0 0 | 01 only
1 0 1 | 0 0 1 0 | 02 only
1 1 1 | 0 0 0 1 | 03 only
comparch@comparchVM:~/comparch/Hw2$ gtkwave decoder_waveform.vcd
```

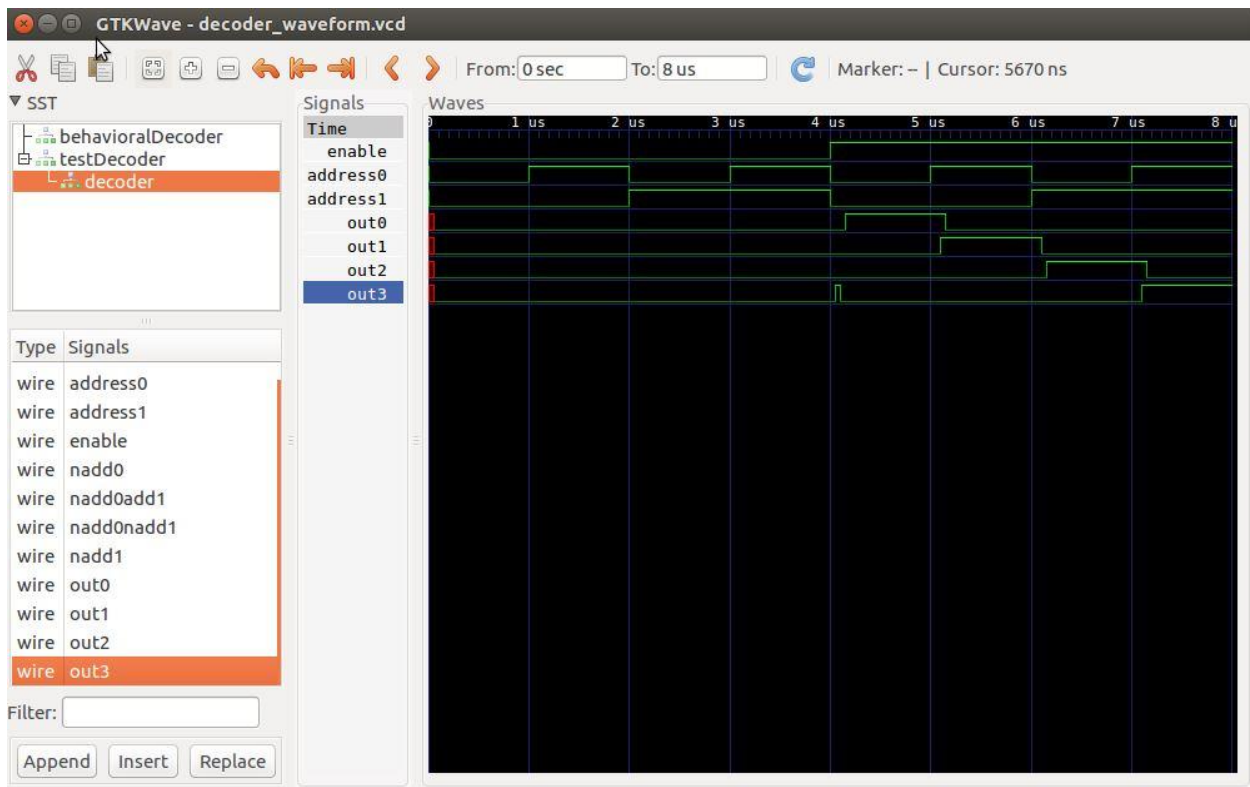


The expected outputs match the actual outputs. The decoder only outputs when enable is on. And it decodes what the binary number is by turning the respective output on.

# Multiplexer

```
comparch@comparchvm:~/comparch/Hw2$ iverilog -o multiplexer multiplexer.t.v
./multiplexer.v:7: warning: timescale for behavioralMultiplexer inherited from another file.
multiplexer.t.v:2: ...: The inherited timescale is here.
./multiplexer.v:20: warning: timescale for structuralMultiplexer inherited from another file.
multiplexer.t.v:2: ...: The inherited timescale is here.
comparch@comparchvm:~/comparch/Hw2$ ./multiplexer
addr1 addr0 | in0 in1 in2 in3 | output | Exp Out
0 0 | 0 0 0 0 | 0 | 0
0 0 | 1 0 0 0 | 1 | 1
0 1 | 0 0 0 0 | 0 | 0
0 1 | 0 1 0 0 | 1 | 1
1 0 | 0 0 0 0 | 0 | 0
1 0 | 0 0 1 0 | 1 | 1
1 1 | 0 0 0 0 | 0 | 0
1 1 | 0 0 0 1 | 1 | 1
```
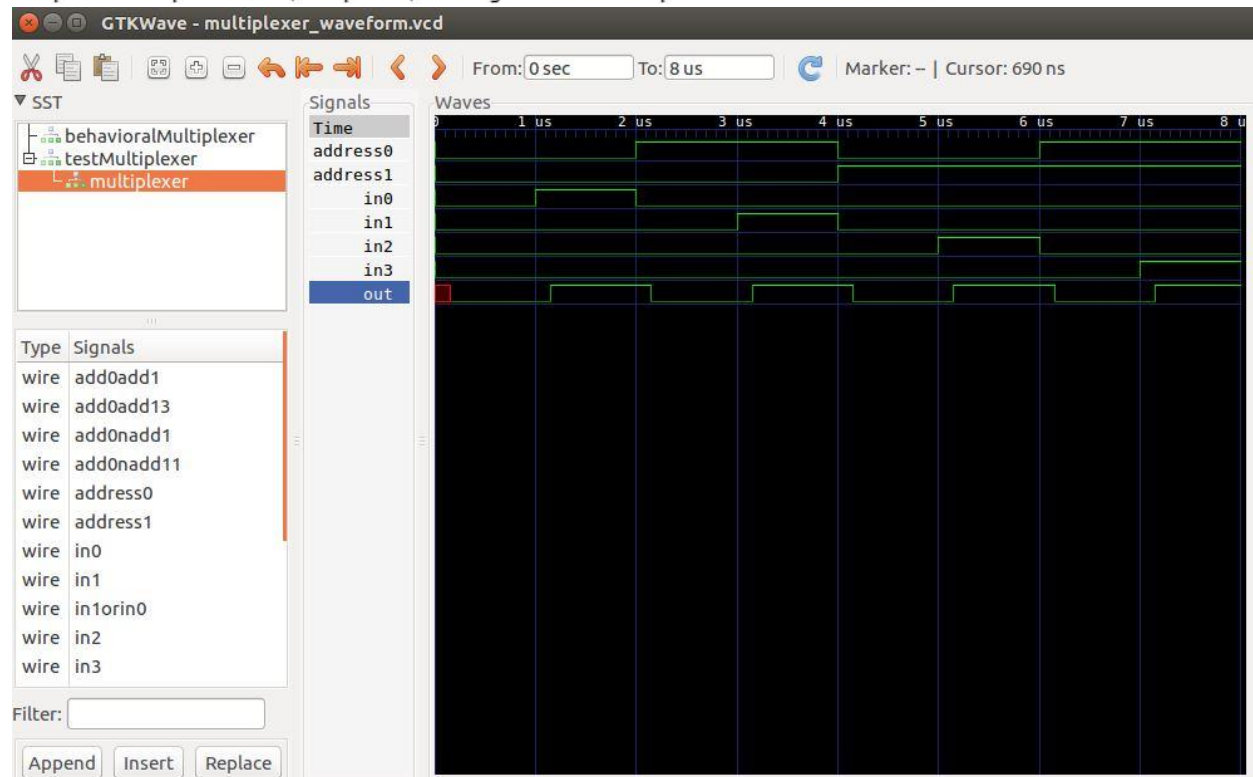
```
comparch@comparchvm:~/comparch/Hw2$ gtkwave multiplexer_waveform.vcd
```



The expected outputs match the actual outputs. The multiplexer uses the address (input) to decide which of the inputs is allowed to go through.